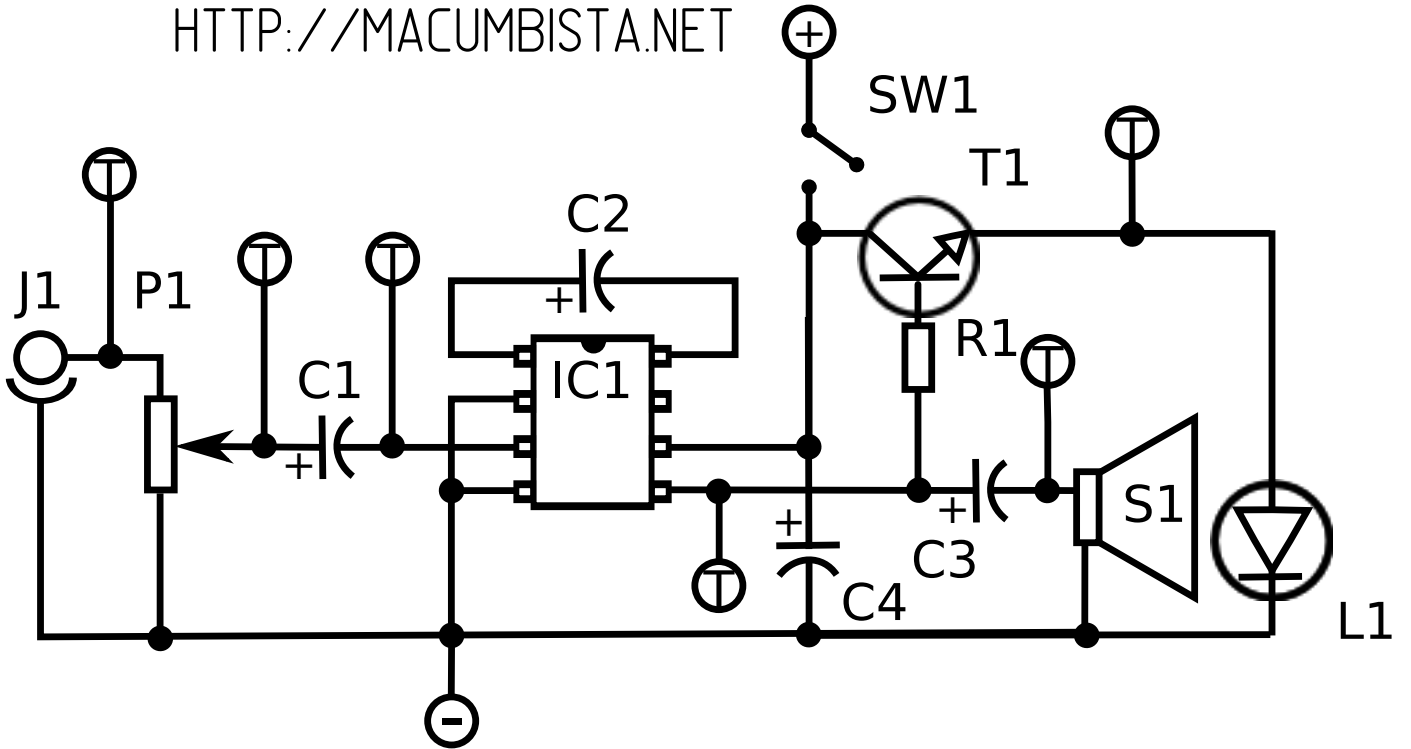


NEANDERTHAL ELECTRONICS SOUNDBOX V 2
[HTTP://MACUMBISTA.NET](http://MACUMBISTA.NET)



P1: 50K Log potenciómetro
 L1: LED
 J1: Neutrik Mono 6,3mm jack
 SW1: SDST/SPDT interruptor
 R1: 1K 1/4W resistencia
 T1: 2N3904 transistor

C1: 1uF condensador
 C2: 10uF condensador
 C3: 100uF condensador
 C4: 1uF condensador
 S1: 1-20W parlante
 IC1: LM386 circuito intergrado de amplificadores

